

## Homework: Ch. 20

1. How is the direction of current flow defined in a conductor? How does this compare to the actual flow?
2. For each quantity below, record the abbreviation, the SI unit, and the unit abbreviation.

<b>Quantity</b>	<b>Quantity Abbreviation</b>	<b>SI unit</b>	<b>Unit Abbreviation</b>
Potential Difference			
Electric Field			
Charge			
Capacitance			
Resistance			
Current			

3. A resistor of  $3.00 \Omega$  is connected in a circuit to a battery of  $2.00 \text{ V}$ . What is the current in the circuit? If you know insert a  $6.00 \text{ V}$  battery into the circuit, what resistance would you need to produce the same amount of current?
4. A common flashlight bulb is rated at  $0.300 \text{ A}$  and  $2.90 \text{ V}$ . If the resistance of the tungsten bulb filament at room temperature ( $20.0 \text{ }^\circ\text{C}$ ) is  $1.10 \Omega$ , what is the temperature of the filament when the bulb is on?
5. When  $115 \text{ V}$  is applied across a wire that is  $10.0 \text{ m}$  long and has a  $0.30 \text{ mm}$  radius, the magnitude of the current  $1.4 \times 10^4 \text{ A}$ . Find the resistivity of the wire.
6. An electrical cable consists of 125 strands of fine wire, each having  $2.65 \mu\Omega$  resistance. The same potential difference is applied between the ends of all the strands and results in a total current of  $0.750 \text{ A}$ .
  - a. What is the current in each strand?
  - b. What is the applied potential difference?
7. A  $120.0 \text{ V}$  potential difference is applied to a space heater whose resistance is  $14.0 \Omega$  when hot. At what rate is electrical energy transferred to thermal energy?

8. An unknown resistor is connected between the terminals of a 3.00 V battery. Energy is dissipated in the resistor at a rate of 0.540 W. The same resistor is then connected between the terminals of a 1.50 V battery. At what rate is the energy now dissipated?
9. A steel trolley car rail has a cross-sectional area of 56.0 cm<sup>2</sup>. What is the resistance of a 10.0 km long rail? Assume that the resistivity of the steel is  $3.00 \times 10^{-7} \Omega \cdot \text{m}$ .
10. A Nichrome heater dissipates 500.0 W when the applied potential difference is 110 V and the wire temperature is 800.0 °C. What would be the dissipation rate if the wire's temperature were held at 200.0 °C? Assume that  $\alpha = 4.0 \times 10^{-4}$  for Nichrome at 800.0 °C.