
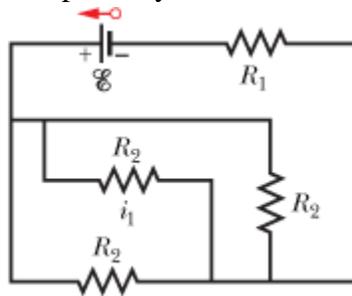


## Homework: Ch. 21

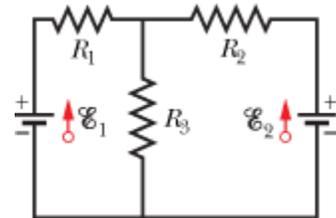1. Describe the behavior of a capacitor in a series RC circuit both right after a potential is applied across it and the resistor and at steady state.
2. A 120 V power line is protected by a 15 A fuse. What is the maximum number of 500 W lamps that can be simultaneously operated in parallel on this line without “blowing” the fuse because of an excess of current?
3. In the figure below,  $R_1 = 6.00 \Omega$ ,  $R_2 = 18.0 \Omega$ , and the ideal battery has emf  $\mathcal{E} = 12.0 \text{ V}$ .
  - a. What is the equivalent resistance?
  - b. How much energy is dissipated by all four resistors in 1.00 min?




4. In the figure on the right, the ideal batteries have emfs  $\mathcal{E}_1 = 10.0 \text{ V}$  and  $\mathcal{E}_2 = 0.500 \mathcal{E}_1$ , and the resistances are each  $4.00 \Omega$ . What is the current in (a) resistance 2 and (b) resistance 3?




5. What multiple of the time constant  $\tau$  gives the time taken by an initially uncharged capacitor in an RC series circuit to be charged to 99.0% of its final charge?

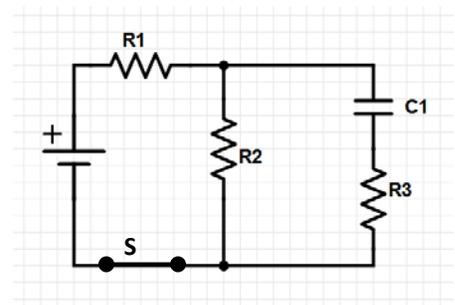6. The figure shows an RC circuit with  $R_1 = 10.0 \Omega$ ,  $R_2 = 15 \Omega$ ,  $R_3 = 5.0 \Omega$ , and capacitance  $C_1 = 10.0 \mu\text{F}$ . The switch  $S$  has been closed for a long enough period that the circuit has reached steady state. Assuming that  $\mathcal{E} = 25 \text{ V}$  and that the battery is ideal, determine the following:




- a. What is the equivalent resistance for this circuit at this time?
- b. What is the voltage and current through  $R_2$ ?
- c. What is the power dissipated by  $R_1$ ?
- d. At time  $t = 0$ , the switch  $S$  is opened. What is the time constant for this circuit?
- e. How long will it take for the current to drop to  $0.5 \text{ A}$ ?

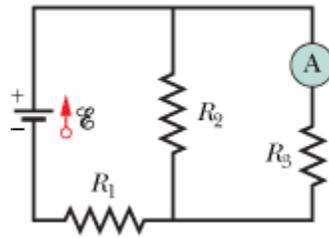7. In the figure below what does the ammeter read if  $\mathcal{E} = 5.0 \text{ V}$  (ideal battery),  $R_1 = 2.0 \Omega$ ,  $R_2 = 4.0 \Omega$ , and  $R_3 = 6.0 \Omega$ ?



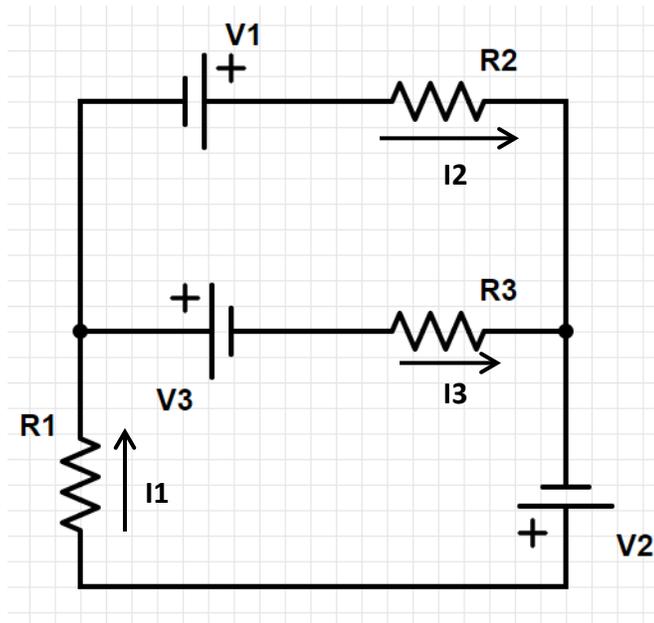8. For the circuit shown below, use Kirchhoff's rules to find the currents  $I_1$ ,  $I_2$ , and  $I_3$ . Assume that batteries are all ideal and have potential  $V_1 = V_2 = 10.0 \text{ V}$  and  $V_3 = 15.0 \text{ V}$ . Also assume that  $R_1 = R_3 = 10.0 \Omega$  and  $R_2 = 20.0 \Omega$ .



9. In an  $RC$  series circuit, emf  $\mathcal{E} = 12.0 \text{ V}$ , resistance  $R = 1.40 \text{ M}\Omega$ , and capacitance  $C = 1.80 \mu\text{F}$ .
- Calculate the time constant.
  - Find the maximum charge that will appear on the capacitor during charging.
  - How long does it take for the charge to build up to  $16.0 \mu\text{C}$ ?
10. A  $15.0 \text{ k}\Omega$  resistor and a capacitor are connected in series, and then a  $12.0 \text{ V}$  potential difference is suddenly applied across them. The potential difference across the capacitor rises to  $5.00 \text{ V}$  in  $1.30 \mu\text{s}$ .
- Calculate the time constant of the circuit.
  - Find the capacitance of the capacitor.