
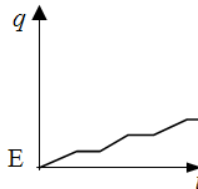
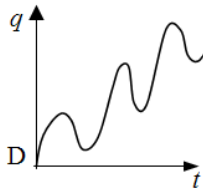
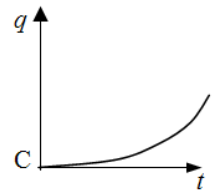
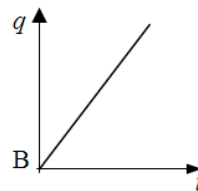


Ch. 21 Worksheet


1. Complete the following statement: The sum of the magnitudes of the currents directed into a junction _____

2. Consider each of the graphs shown. Which of these graphs represents the charge on a capacitor as it is being charged in a circuit containing a resistor and a capacitor in series shortly after they are connected to a battery?

- a. A
- b. B
- c. C
- d. D
- e. E

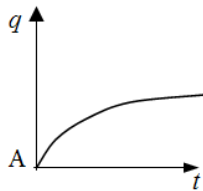

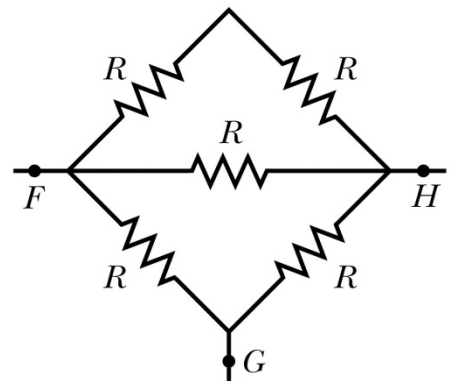3. The figure to the right shows five $5.00\ \Omega$ resistors. Find the equivalent resistance between points F and H . (Hint: For each pair of points, imagine that a battery is connected across the pair.)



4. A car battery with a 12 V emf and an internal resistance of $0.040\ \Omega$ is being charged with a current of 50 A. What are (a) the potential difference across the terminals, (b) the rate P_r of energy dissipation inside the battery, and (c) the rate P_{emf} of energy conversion to chemical form?

5. In the figure below, the resistance of the each resistor is $R_1 = R_2 = R_3 = 2.00\ \Omega$, $R_4 = 16.0\ \Omega$, $R_5 = 8.00\ \Omega$, and $R_6 = 4.00\ \Omega$. What is the equivalent resistance?

