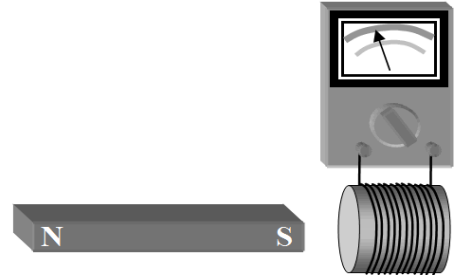


## Ch. 23 Worksheet


1. An ammeter is connected to a coil of wire. A magnet is sitting motionless next to the coil and perpendicular to the plane of the coil as shown. The meter indicates that a current is flowing through the wire from the left toward the right. What, if anything, is wrong with this picture?

- The current should be flowing from the right toward the left.
- The needle should be slanted toward the right.
- The needle should indicate that there is no current flowing.
- There is nothing wrong with the picture.



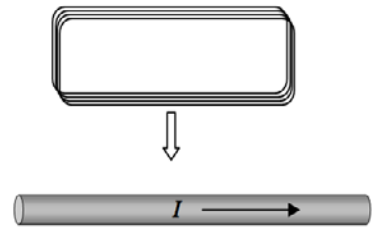2. A coil of wire that forms a complete loop is moving with a constant speed  $v$  toward a very long, current carrying wire, only a portion of which is shown. What affect, if any, does the current carrying wire have on the coil of wire?

- Since the magnetic field increases as the coil approaches the wire, a current is induced in the coil.
- The rectangle will be distorted as it is pulled in the direction of the current in the wire.
- Close to the wire, a magnetic force acts on the loop that accelerates the loop away from the wire.
- Since the magnetic field around the wire is not changing, there is no effect on the coil.
- Since the coil and the wire are not touching, there is no effect.



3. A small loop of area  $6.8 \text{ mm}^2$  is placed inside a long solenoid that has 854 turns/cm and carries a sinusoidally varying current  $i = 1.28 \text{ A}$  and angular frequency 212 rad/s. The central axes of the loop and the solenoid coincide. What is the amplitude of the emf induced in the loop?

4. A solenoid having an inductance of  $6.30 \mu\text{H}$  is connected in series with a  $1.20 \text{ k}\Omega$  resistor. If the  $14.0 \text{ V}$  battery is connected across the pair, how long will it take for the current through the resistor to reach  $80.0\%$  of its final value?

5. A coil of inductance  $88 \text{ mH}$  and unknown resistance and a  $0.94 \mu\text{F}$  capacitor are connected in series with an alternating emf of frequency  $930 \text{ Hz}$ . If the phase constant between the applied voltage and the current is  $75^\circ$ , what is the resistance of the coil?

6. An oscillating LC circuit has a current of 7.50 mA, potential difference amplitude of 250 mV, and a capacitance of 220 nF. Determine the following:
- maximum energy stored in the capacitor
  - maximum energy stored in the inductor
  - period of oscillation
  - the inductance in  $\mu\text{H}$